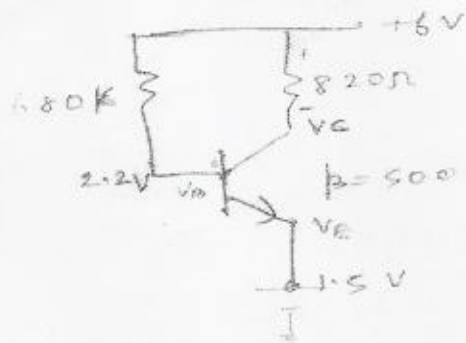


BJT



$$I_B = \frac{6 - 2.2}{680K}$$

$$= \underline{5.58 \mu A}$$

$$I_C = \beta I_B$$

$$= 500 \times 5.58 \mu A$$

$$= \underline{2.79 mA}$$


$$V_C = 6 - 820 \times 2.79 \times 10^{-3}$$

$$V_C = 3.708V$$

$$V_{CE} = 3.708 - 1.5$$

$$= \underline{2.208V}$$

$$(V_{CE}, I_C) = (2.208V, 2.79mA)$$

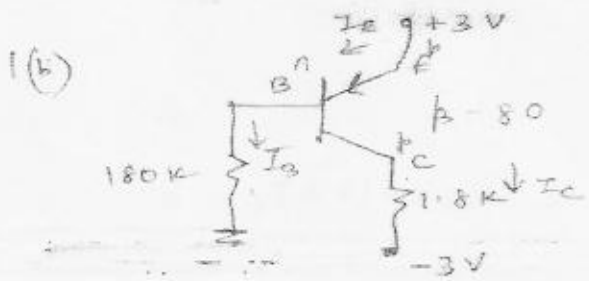

$$V_B = 2.3V$$

$$I_B = \frac{2.3}{180K}$$

$$= \underline{12.77 \mu A}$$

$$I_C = \beta I_B$$

$$= \underline{1.02 mA}$$


$$I_C = \frac{V_C - (-3)}{1.8K}$$

$$1.02 mA \times 1.8K - 3 = V_C$$

$$V_C = -1.164V$$

$$V_{CE} = -4.164V$$

2.

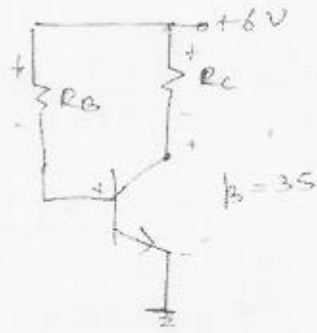

$$V_{CE} = 3V$$

$$I_C = 0.5 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = 0.0143 \text{ mA}$$

$$6 - I_C R_C - V_{CE} = 0$$

$$6V - I_B R_B - 0.7 = 0$$

$$6 - 0.5 \text{ mA} \times R_C - 3 = 0$$

$$5.3 - I_B R_B$$

$$0.5 \text{ mA} \times R_C = 3$$

$$R_B = \frac{5.3}{0.0143} \times 10^3$$


$$R_C = \frac{3}{0.5} \times 10^3$$

$$0.0143$$

$$R_C = 6 \text{ k}\Omega$$

$$R_B = 370.629 \text{ k}\Omega$$

3.

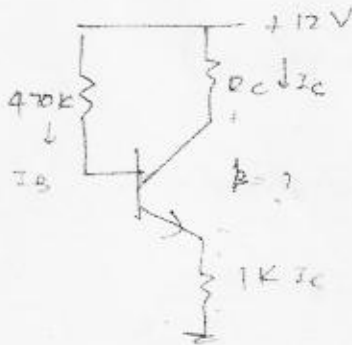

$$V_{CE} = 4V$$

$$I_C = 2 \text{ mA}$$

$$R_C \ll \beta$$

$$12 - I_C R_C - V_{CE} - 1k \times I_E = 0$$

$$12 - 470k \times I_B - 0.7 - 1k \times I_E = 0$$

$$I_C = \beta I_B = 2 \text{ mA}$$

$$I_B = \frac{2 \text{ mA}}{\beta}$$

$$I_E = (\beta + 1) I_B$$

$$= \left(\frac{\beta + 1}{\beta} \right) 2 \text{ mA}$$

$$12 - 2 \text{ mA} \times R_C - 4 - 1k \times \left(\frac{\beta + 1}{\beta} \right) 2 \text{ mA} = 0$$

$$12 - 470k \times \frac{2 \text{ mA}}{\beta} - 0.7 - 1k \times \left(\frac{\beta + 1}{\beta} \right) 2 \text{ mA} = 0$$

$$8 - 2 \text{ mA} \times R_C - 2 \times \left(\frac{101.86}{100.86} \right) = 0$$


$$8 - 2 \text{ mA} \times R_C - 2 \left(\frac{\beta + 1}{\beta} \right) = 0$$

$$8 - 2 \times \left(\frac{101.86}{100.86} \right) = 2 \text{ mA} \times R_C$$

$$11.3 - \frac{940}{\beta} - 2 \left(\frac{\beta + 1}{\beta} \right) = 0$$

$$11.3k - 940 - 2\beta - 2 = 0$$

4.

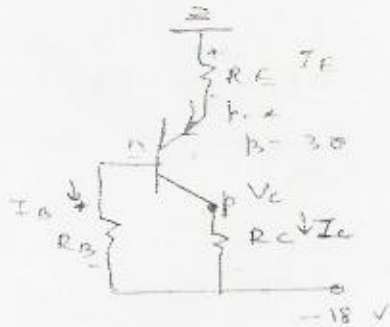

$$V_{CE} = -8V$$

$$I_C = 2mA$$

$$V_C = -12V$$

$$\frac{V_C - (-18)}{R_C} = I_C$$

$$R_C = \frac{V_C + 18}{2mA}$$

$$= \frac{6}{2mA} = \underline{\underline{3K\Omega}}$$

$$I_B = \frac{I_C}{\beta} = \frac{2mA}{30} = 0.0666mA$$

$$I_E = 2.066mA$$

$$-I_E R_E - 0.7 - I_B R_B + 18 = 0$$

$$V_{CE} = V_C - V_E$$

$$-8 = -12 - V_E$$

$$\underline{\underline{V_E = -4V}}$$

$$R_E = \frac{0 - (-4)}{I_E} = \frac{4}{2.066mA}$$


$$= \underline{\underline{1.94K\Omega}}$$

$$-2.066 \times 10^{-3} \times 1.936 \times 10^3 - 0.7 - 0.0666 \times 10^{-3} \times R_B + 18 = 0$$

$$13.3 = 0.0666 \times 10^{-3} \times R_B$$

$$\underline{\underline{R_B = 199.7K\Omega}}$$


5.

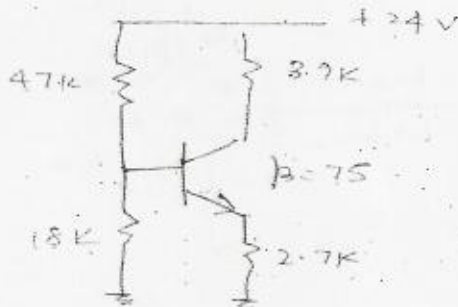

$$V_{Th} = \frac{24 \times 18}{47 + 18}$$

$$= \underline{\underline{6.646V}}$$

$$R_{Th} = 13.0153K\Omega$$

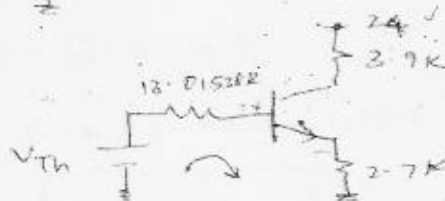

$$6.646 - 13.01538 \times I_B - 0.7 - 2.7 \text{ k} \times 76 \times I_B = 0$$

$$5.946 = I_B (13.01538 + 205.2 \text{ k})$$

$$I_B = 27.25 \mu\text{A}$$

$$I_C = 2.043 \text{ mA}$$


$$I_E = 2.071 \text{ mA}$$

$$24 - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = 24 - 2.043 \text{ mA} \times 3.9 \times 10^3 - 2.071 \times 10^{-3} \times 2.7 \text{ k}$$

$$V_{CE} = 10.4406 \text{ V}$$

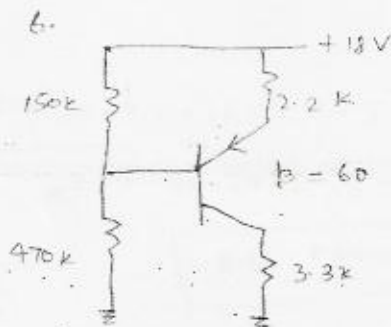
$$(V_{CE}, I_C) = (10.44 \text{ V}, 2.043 \text{ mA})$$



$$V_{Th} = \frac{18 \times 470}{470 + 150}$$

$$= 13.645 \text{ V}$$

$$R_{Th} = 113.7096 \text{ k}$$

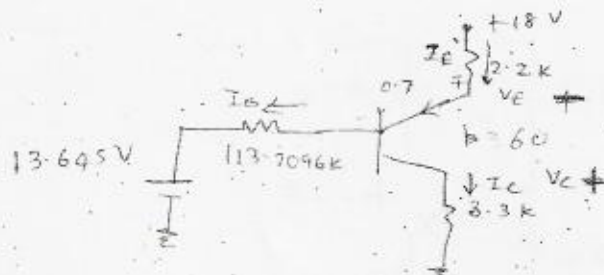


$$18 - I_E \times 2.2 \text{ k} - 0.7 - 113.7096 \text{ k} \times I_B - 13.645 \text{ V} = 0$$

$$3.655 = (61 \times 2.2 \text{ k} + 113.7096 \text{ k}) I_B$$

$$I_B = 4.74 \mu\text{A}$$

$$I_E = 0.9 \text{ mA}$$

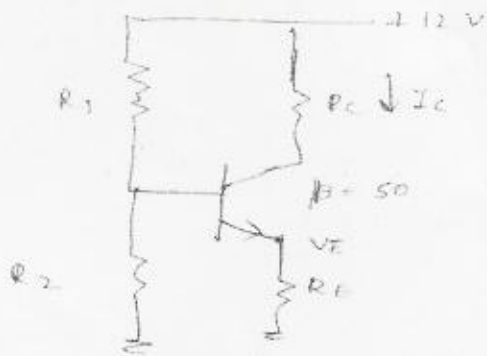

$$V_{CE} = 4V$$

$$I_C = 1.5 \text{ mA}$$

$$R_E = 1.5 \text{ k}$$

$$V_E = I_E R_E$$

$$V_E = \frac{I_C (\beta + 1) \times 1.5 \text{ k}}{\beta}$$

$$= \frac{1.5 \times 1.5 \times 51}{50}$$

$$V_E = 2.295 \text{ V}$$


$$V_{CE} = 4 = V_C - V_E$$

$$V_C = 6.295 \text{ V}$$

$$I_C = \frac{12 - 6.295}{R_C}$$

$$R_C = \frac{12 - 6.295}{1.5 \text{ mA}}$$

$$R_C = 3.803 \text{ k}$$

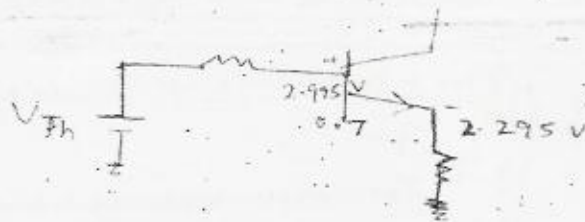

IRPAK

$$I_B = \frac{V_{th} - 2.295}{R_B}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_B = 30 \mu\text{A}$$

$$I_B \times \frac{R_1 R_2}{R_1 + R_2} = \frac{12 \times R_2}{R_1 + R_2} - 2.295$$

Assume $R_B = 100 \text{ k}$

$$30 \mu\text{A} \times 100 \text{ k} + 2.295 = V_{th}$$

$$V_{th} = 5.995 \text{ V}$$

$$100K = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_1 + R_2 = \frac{R_1 R_2}{100K}$$



$$5.995 = \frac{12 R_2}{R_1 + R_2}$$

$$5.995 = \frac{12 R_2}{R_1 + 0.2}$$


$$R_1 + R_2 = \frac{12 R_2}{5.995}$$

$$100K = \frac{R_1 R_2 \times 5.995}{12 R_2}$$

$$R_1 = \frac{100K \times 12}{5.995}$$


$$R_2 \approx 200K\Omega$$

$$R_1 = 200.166K\Omega$$

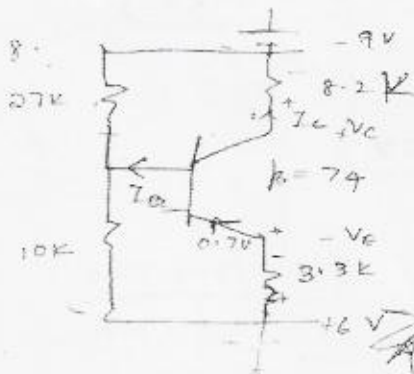

$$-9V + 8.2K I_{C} - V_{CE} + 3.3K I_{E} - 6V = 0$$
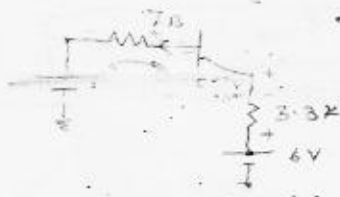
$$V_{CE} = -15 + 8.2K I_{C} + 3.3K I_{E}$$



$$0 = V_{th} + I_{B} R_{B} + 0.7V + 3.3K I_{E} - 6V = 0$$

$$\frac{10 \times -9}{37} + I_{B} (7.297K + 3.3K \times 75) - 5.3 V_{th} = 0$$

$$R_B = \frac{10 \times 27}{37} = 7.297K\Omega$$

$$\frac{27 \times +6}{37} = I_{B} = \frac{5.3 + 4.05}{7.297K + 3.3K \times 75}$$

$$I_E = 75 I_B$$


$$I_B = 36.7\mu A$$

$$V_{th} = \frac{+15 \times 27}{37}$$


$$= 10.9V$$

$$I_C = 2.715mA$$

$$I_E = 2.752mA$$

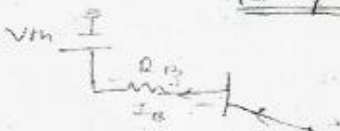
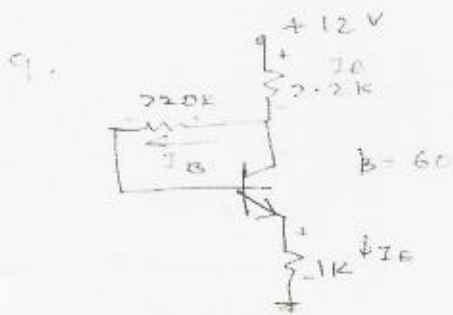
$$V_{CE} = -15 + 8.2K \times 2.715mA + 3.3K \times 2.752mA$$



$$12 - I_B \times 220k - 0.7 - 60 I_B = 0$$

$$11.3 = I_B (220k + 60 \times 1k)$$

$$I_B = 40.21 \mu A$$


$$I_C = 2.4128 mA$$

$$I_E = 2.453 mA$$

$$12 - 2.2k \times 2.453 - V_{CE} - 1k \times 2.453 = 0$$

$$V_{CE} = 12 - 2.2 \times 2.453 - 2.453$$

$$V_{CE} = 4.15V$$

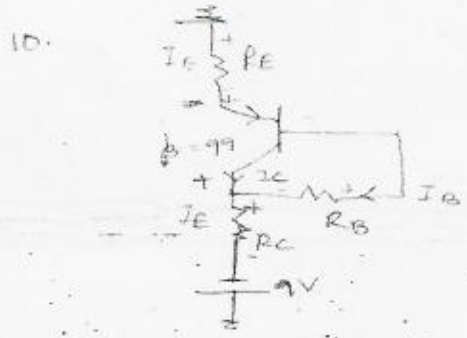

$$-I_E R_E - 0.7 - I_B R_B - I_C R_C = 0$$

$$8.3 = 100 I_B R_E + I_B R_B + 100 I_B R_C$$

$$-I_E R_E + V_{CE} - I_C R_C + 9V = 0$$

$$V_{CE} = -3V$$

$$I_C = 1.98 mA$$

$$I_B = 20 \mu A$$

$$I_E = 2 mA$$

$$V_E = -3V$$


$$R_E = \frac{0 - V_E}{I_E} = \frac{3}{2mA} = 1.5k\Omega$$

$$-2 \times 10^{-3} \times 1.5k + (-3V) - 2mA \times R_C = 0$$

$$3 = 2mA \times R_C$$

$$R_C = 1.5k\Omega$$
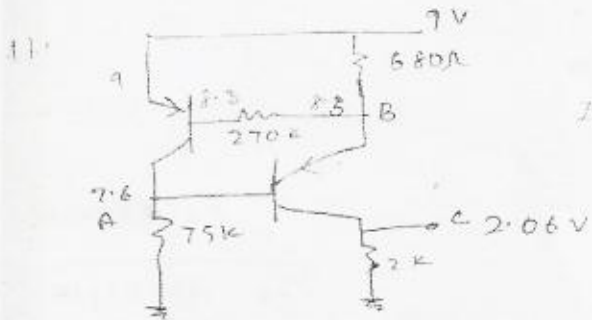
$$8.3 = 100 \times 20 \mu A \times 1.5k + 20 \mu A \times R_B + 100 \times 20 \mu A \times 1.5k$$





$$I_E = 1.03 \text{ mA}$$

$$V_B = 8.3 \text{ V}$$

$$V_C = 2.06 \text{ V}$$

$$V_A = 7.6 \text{ V}$$

12. $\beta = \infty$

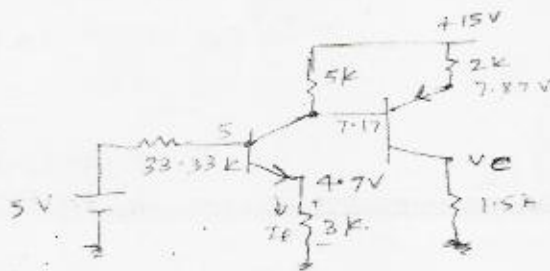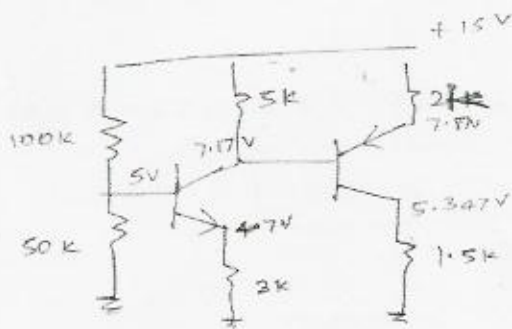

$$I_B = 0$$

$$I_{E1} = \frac{4.7}{3 \text{ k}} = 1.566 \text{ mA}$$

$$I_{C1} = 1.566 \text{ mA}$$



$$V_C = 15 - 1.566 \times 5 = 7.87 \text{ V}$$

$$I_{E2} = \frac{15 - 7.87}{2 \text{ k}} = 3.565 \text{ mA}$$

$$I_{C2} = 3.565 \text{ mA}$$

$$V_C = 3.565 \times 1.5 = 5.3475 \text{ V}$$

13.

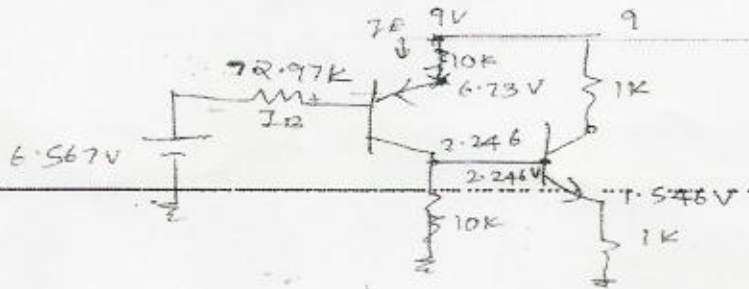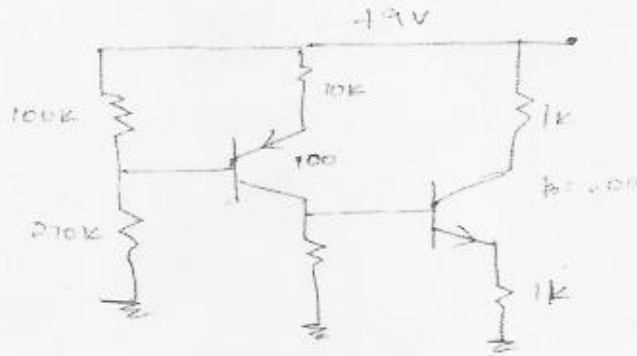

$$9V - 10K \times I_E - 72.97K \times I_B - 6.567V = 0$$

$$2.433V = 10K \times 101 I_B + 72.97K \times I_B$$

$$I_B = \frac{2.433}{(10 \times 101 + 72.97)K}$$

$$I_B = 2.246 \mu A$$

$$I_E = 0.227 mA$$

$$I_C = 0.2246 mA$$


$$I_{E2} = \frac{1.546}{1K} = 1.546 mA$$

$$I_{C2} = 1.5308 mA$$

$$V_C = 9 - 1.5308 mA \times 1K$$

$$= 7.47V$$

$$V_{CE} = 5.924V$$

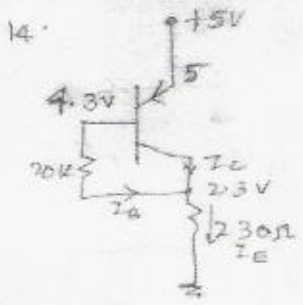

$$I_E = \frac{2.3}{230}$$

$$= 10 \text{ mA}$$



$$I_B = \frac{2}{20k}$$

$$= 0.1 \text{ mA}$$

$$I_E = (\beta + 1) I_B$$

$$10 = (\beta + 1) 0.1$$

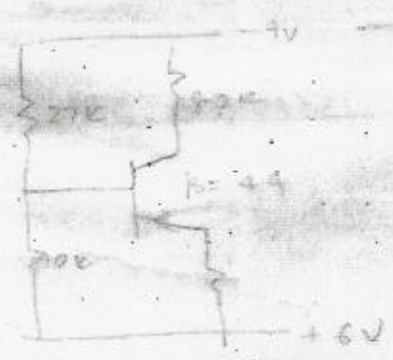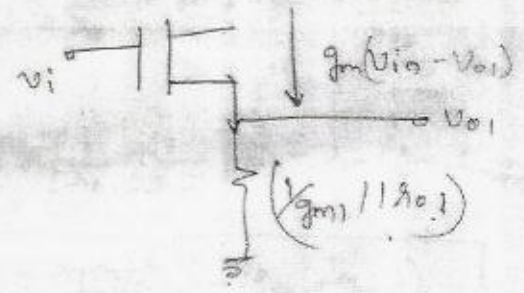
$$\beta + 1 = 100 \quad \boxed{\beta = 99}$$



$$R_{in} = \frac{270}{27} \cdot \frac{-9.10}{37}$$

$$= -2.43 \text{ V}$$


$$= 7.297k$$

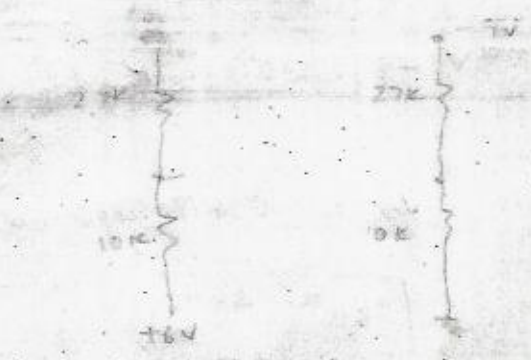

$$\frac{6 \times 27}{37} = 4.378 \text{ V}$$

$$V_{o1} = 4.378 - 2.43$$

$$= 1.945 \text{ V}$$

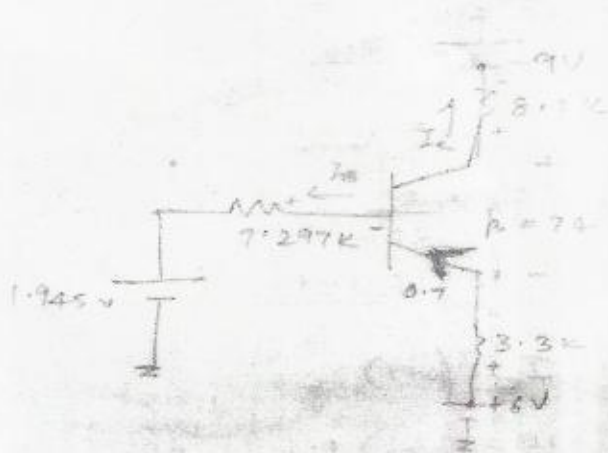

$$1.945 + 7.297k I_B + 0.7 + 3.3k \times 75 I_B - 6 = 0$$

$$7.297k I_B + 3.3k \times 75 I_B = 5.3 - 1.945$$

$$I_B = \frac{3.355}{(7.297 + 3.3k \times 75)}$$

$$I_B = 13.16 \mu A$$

$$I_C = 0.974 \text{ mA}$$

$$-9V + 8.2k \times 0.974 \text{ mA} - V_{CE} + 3.3k \times 0.987 \text{ mA} - 6V = 0$$

$$V_{CE} = -15 + 7.9868 + 3.257$$

$$V_{CE} = -3.7561V$$