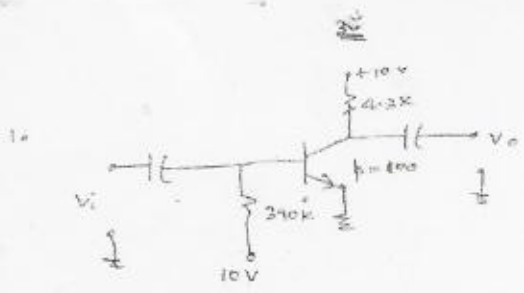


143



$I_B, I_C \text{ \& } r_e$:

$$10 - 4.3k I_C - V_{CE} = 0$$

$$10 - 390k \times I_B - 0.7 = 0$$

$$9.3 = 390k \times I_B \quad I_B = \frac{9.3}{390k}$$


$$I_B = 23.85 \mu A$$

$$I_C = \beta I_B = 2.38 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 2.41 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \frac{26 \text{ mV}}{2.4 \text{ mA}} = 10.83 \Omega$$

Eq.ckt

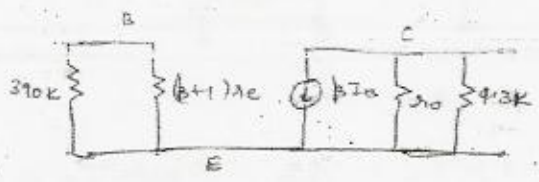

(i) $r_o = \infty$

$$Z_i = 390k \parallel (\beta + 1) r_e = 390k \parallel 101 \times 10.83 \Omega$$

$$= 390k \parallel 1.094k = 1.091k$$

$$Z_{out} = 4.3k$$

$$A_{v_c} = -\frac{4.3k}{10.83} = -397.04$$

(ii) $R_o = 50K$

$Z_{in} = 1.091K$

$$Z_{out} = 50K \parallel 4.3K$$

$$= \underline{3.96K}$$

$$A_v = - \frac{3.96K}{10.88} = \underline{-365.65}$$

(iii) $R_o = 20K$


$Z_{in} = 1.091K$

$$Z_{out} = 20K \parallel 4.3K$$

$$= \underline{3.54K}$$

$$A_v = - \frac{3.54K}{10.88} = \underline{-326.78}$$

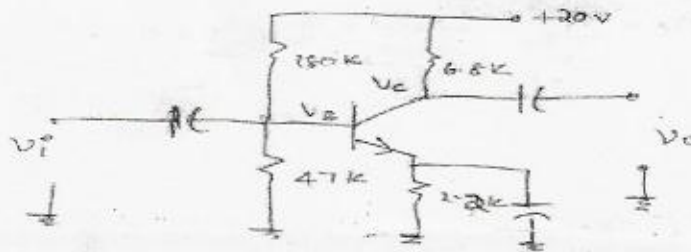
2. $V_B, V_C, I_E, Z_i, Z_o, A_v, R_o = 50K, \beta = 120$



$$20 - 6.8 \times I_C - V_{CE} - 2.2K \times I_E = 0$$

$$V_E = \frac{47 \times 20}{(150 + 47)} = 4.14V$$

$$R_T = 37.27K\Omega$$

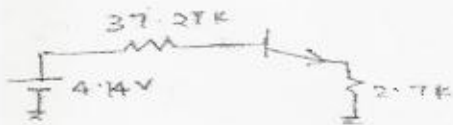

$$4.14 - 37.27K I_B - 0.7 - 121 I_B \times 2.2K = 0$$

$$4.14 - 0.7 = (37.27K + 121 \times 2.2K) I_B$$

$$I_B = \underline{11.33 \mu A}$$

$$I_C = 1.36 \text{ mA}$$

$$I_E = 1.37 \text{ mA}$$

$$V_E = I_E R_E = 1.37 \times 2.2 = 3.014 \text{ V}$$

$$V_B = \underline{3.714 \text{ V}}$$

$$\frac{20 - V_C}{6.8K} = 1.36 \text{ mA}$$

$$V_C = 20 - 6.8 \times 1.36 = \underline{10.752 \text{ V}}$$

$$Z_i = R_B \parallel (\beta + 1) r_e$$

$$= 37.27K \parallel (121) \times r_e$$

$$= 37.27K \parallel 2.3K$$

$$= \underline{2.17K}$$

$$r_e = \frac{26 \text{ mV}}{1.37 \text{ mA}}$$

$$= 18.97 \Omega$$


$$(\beta + 1) r_e = 2.3K$$

$$Z_{out} = R_C \parallel r_o$$

$$= 6.8K \parallel 50K = \underline{5.986K}$$

$$A_v = -\frac{R_C'}{r_e} = -\frac{5.986K}{18.97} = \underline{-315.55}$$

3.

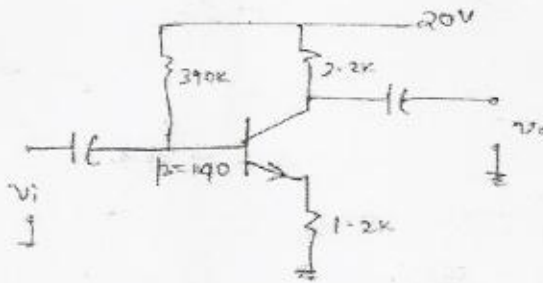

r_e, Z_i, Z_o, A_v

$r_o(i) 100k$

(ii) 20k

$$20 - 2.2 \times I_C - V_{CE} - 1.2k \times I_E = 0$$

$$20 - 390k \times I_B - 0.7 - 1.2k \times 141 \times I_B = 0$$


$$\therefore 19.3 = I_B (390k + 1.2k \times 141)$$

$$I_B = \frac{19.3}{(390 + 1.2 \times 141)k}$$

$$= \underline{34.5 \mu A}$$

$$I_E = \underline{4.87 mA}$$
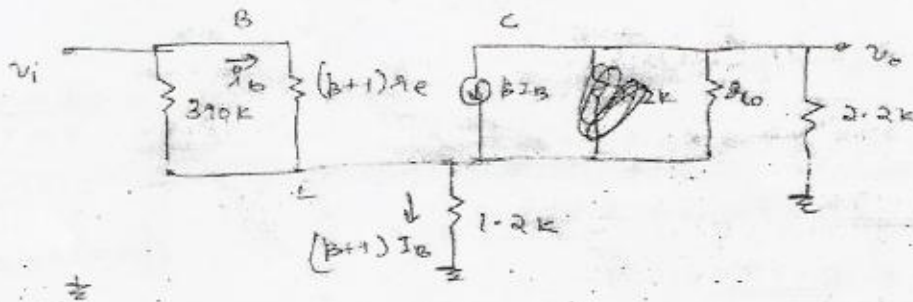
$$r_e = \frac{26mV}{4.87mA} = \underline{5.34 \Omega}$$





$$(\beta+1)r_e = 5.34 \times 141$$

$$= \underline{752.94 \Omega} \quad 11390k \approx 752.94k$$

$$v_i = r_b [R_B \parallel (\beta + 1)r_e] + (\beta + 1)I_B R_E$$

~~$$v_o = \dots$$~~

$$Z_{in} = R_B \parallel (Z_{in})$$

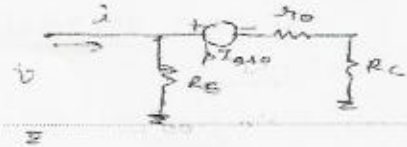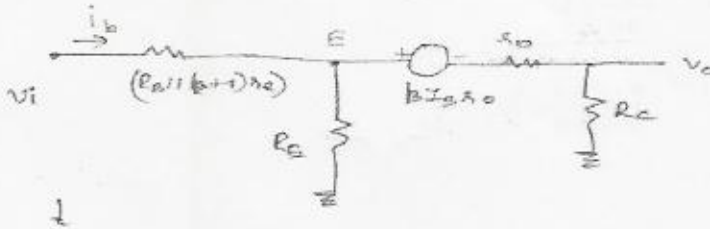

~~$$Z_{in} = (R_B \parallel (\beta + 1)r_e) + R_E \left(1 + \frac{\beta}{1 + \frac{R_C + R_C}{r_o}} \right)$$~~



~~$$\frac{v_o}{v_{in}} = -\frac{R_C}{R_E} \left(\frac{1}{1 + \frac{R_C + R_C}{\beta r_o}} \right)$$~~

$$\beta I_B r_o - i r_e - i r_e - i r_o = 0$$

$$\beta I_B r_o = i (R_E + R_C + r_o)$$

$$v = i R_E \quad i =$$

$$v = I \quad I_B = i \left(\frac{R_E + R_C + r_o}{\beta r_o} + \frac{1}{\beta} \right)$$

$$i = \frac{\beta I_B r_o}{R_E + R_C + r_o}$$

$$i = \frac{\beta I_B}{\left(\frac{R_E + R_C}{r_o} + 1 \right) + \frac{1}{\beta}}$$

$$i = I_B \left[\frac{\beta}{\left(\frac{R_E + R_C}{r_o} + 1 \right) + \frac{1}{\beta}} \right]$$

$$v = (\beta + 1) I_B R_E \left[\frac{\beta}{\left(\frac{R_E + R_C}{r_o} + 1 \right) + \frac{1}{\beta}} \right]$$

$$R_E \left(1 + \frac{\beta}{1 + \frac{R_E + R_C}{r_o}} \right)$$

$$R_E' = 1.2k \parallel 752.94\Omega$$

$$= 1.2k \parallel 0.753k$$

$$= 0.463k$$

$$r_o = 100k$$

$$Z_{in} = 752.94\Omega + 1.2k \left(1 + \frac{140}{1 + \frac{1.2 + 2.2}{100}} \right)$$

$$= 752.94\Omega + 1.2k \left(1 + \frac{140}{1.034} \right)$$

$$= \underline{164.4k\Omega}$$

$$r_o = 20k$$

$$Z_{in} = 752.94\Omega + 1.2k \left(1 + \frac{140}{1 + \frac{1.2 + 2.2}{20}} \right)$$

$$= \underline{145.54k\Omega}$$

$$r_o = 100k$$

$$Z_{out} = R_E' + r_o \left(1 + \frac{R_C}{r_o} \right)$$

$$r_o = 20k$$

$$= R_E' + r_o \left(1 + \frac{R_E'}{r_e} \right)$$

$$= 0.463 + 20 \left(1 + \frac{0.463}{0.005} \right)$$

$$= \underline{1.872 \text{ M}\Omega}$$

Gain:

$$r_o = 100k$$

$$A_v = -\frac{R_C}{R_E} \left(\frac{1}{1 + \frac{R_E + R_C}{\beta r_o}} \right)$$

$$= -\frac{2.2}{1.2} \left(\frac{1}{1 + \frac{1.2 + 2.2}{140 \times 100k}} \right)$$


$$= \underline{-1.83}$$

$$r_o = 20k$$

$$= -\frac{2.2}{1.2} \left(\frac{1}{1 + \frac{1.2 + 2.2}{140 \times 20k}} \right)$$

$$= \underline{-1.83}$$

4. r_e, Z_i, A_v $r_o = 10k\Omega$

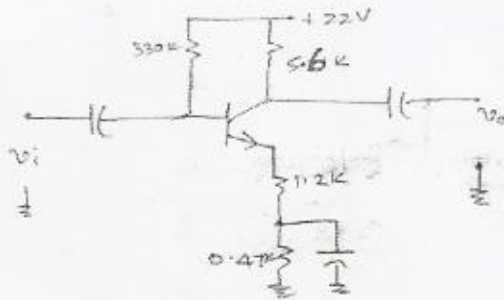

$$22 - 5.6 \times I_C - V_{CE} - I_E \times 1.67 = 0$$

$$22 - I_B \times 330 - 0.7 - \beta I_B \times 1.67 = 0$$

$$21.3 = I_B (330 + \beta \times 1.67) k$$

$$I_B = 45.77 \mu A$$

$$I_E = 8.7 mA$$

$$r_e = \frac{V_T}{I_E} = \frac{26}{8.7} = 7.02 \Omega$$

$R_B \parallel$

$$Z_i = \left(R_B \parallel (\beta + 1) r_e \right) + R_E \left(1 + \frac{\beta}{1 + R_E + R_C} \right)$$


$$Z_i = 81 \times 7.02 \Omega + 1.2 k \left(1 + \frac{80}{1 + 1.2 + 5.6} \right)$$

$$= 83.82 k \Omega \parallel 330 k = 66.84 k \Omega$$

$$A_v = - \frac{R_C}{R_E} \left(\frac{1}{1 + \frac{R_E + R_C}{\beta r_e}} \right) = - \frac{5.6}{1.2} \left(\frac{1}{1 + \frac{6.8}{80 \times 7.02}} \right)$$

$$A_v = -4.656$$

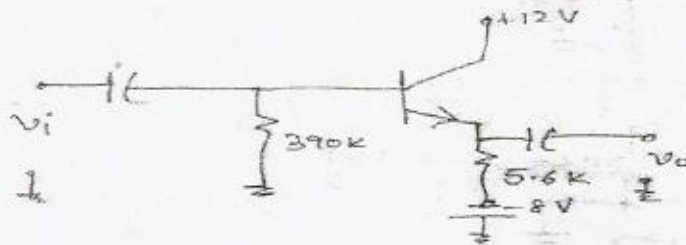5. Z_i, Z_o, A_v $\beta = 120$ $r_o = 40 \text{ k}$



$$-I_b \times 390 \text{ k} - 0.7 - 121 I_b \times 5.6 + 8 = 0$$

$$7.3 = I_b (12 \times 5.6 + 390) \text{ k}$$

$$I_b = \frac{7.3}{(12 \times 5.6 + 390) \text{ k}}$$

$$= 6.84 \mu\text{A}$$

$$I_E = 0.83 \text{ mA}$$

$$r_e = \frac{26}{0.83} = 31.325 \Omega$$

$$Z_i = \left[R_B \parallel (R_{B1} + r_e) \right] + R_E \left(1 + \frac{\beta}{1 + \frac{R_E}{r_o}} \right)$$

$$= \left[12 \times 31.325 + 5.6 \right] \left(1 + \frac{120}{1 + \frac{5.6}{40}} \right)$$

$$= 592.86 \text{ k}\Omega$$

$$Z_{o1} = R_C' + r_o \left(1 + \frac{R_C'}{r_e} \right)$$

$$= 5.26 \text{ k} + 40 \left(1 + \frac{2.26 \text{ k}}{0.0312} \right)$$

$$R_C' = R_C \parallel R_L$$

$$= 5.6 \text{ k}$$

$$= 5.6 \text{ k}$$

$$= 2.26 \text{ k}$$

$$R_E' = R_E \parallel R_o$$

$$= 5.6 \parallel 140k$$

$$= \underline{4.91k}$$

$$r_e = 31.325\Omega$$

$$A_v = \frac{4.91k}{0.031 + 4.91} = \frac{4.91}{4.91 + 0.031} = \underline{0.994}$$

I_b R_s in series

$$r_e + \frac{R_s \parallel 1390k}{(\beta + 1)}$$

$$Z_{in} = \left[\frac{R_B + r_e}{\beta + 1} \parallel R_E \right] + (\beta + 1)(r_e')$$

$$= \left[\frac{121k + 31.325\Omega \parallel 1390k}{121} \right] + (121) \times 4.91k$$

$$= \left[\frac{3.79k \parallel 1390k}{121} \right] + 594.11k$$

$$= \underline{597.89k} \quad (\beta + 1)(r_e + R_E') \parallel R_B$$

$$\frac{R_B + r_e}{\beta + 1} \parallel R_E'$$

$$= 121(31.325 + 4.91k) \parallel 1390k$$

$$= 597.89 \parallel 1390k$$


$$= \underline{235.89k}$$

$$= 31.325 \parallel 4.91k$$

$$= 0.031k \parallel 4.91k$$

$$= 0.0308k$$

$$= \underline{30.8\Omega}$$

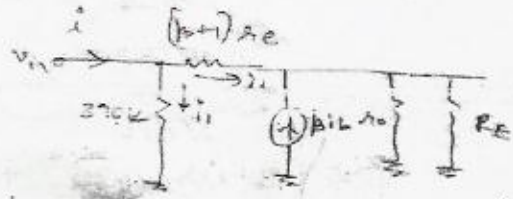


6. $I_b, I_c, r_e, Z_i, Z_o, A_v$

$$i = i_b + i_e$$


$$\frac{v_{in}}{Z_{in}} = \frac{v_{in}}{R_B} + \frac{v_{in}}{(\beta + 1)(r_e + R_E')}$$
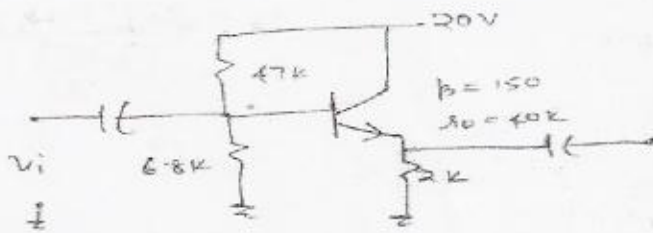
$$Z_{in} = R_B \parallel (\beta + 1)(r_e + R_E')$$



$$V_T = \frac{6.8 \times 20}{6.8 + 47}$$

$$= 2.52 \text{ V}$$

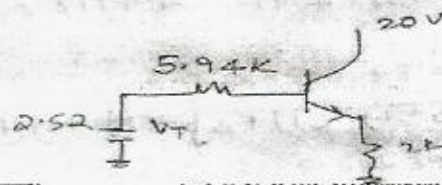

$$2.52 - I_B \times 5.94 \text{ k} - 0.7 - 151 I_B \times 2 \text{ k} = 0$$

$$1.82 = I_B (5.94 \text{ k} + 151 \times 2)$$

$$I_B = 5.91 \mu\text{A}$$

$$I_C = 0.886 \text{ mA}$$

$$I_E = 0.892 \text{ mA}$$

$$r_c = \frac{V_T}{I_E} \approx \frac{26}{0.892} = 29.15 \Omega$$

$$Z_i = \left[(151 + 1) r_c + (151 + 1) [R_E \parallel R_L] \right] \parallel R_B$$

$$R_E \parallel R_L = 2 \text{ k} \parallel 40 \text{ k} = 1.9 \text{ k} \quad [4.4 \text{ k} + 151 \times 29.15 \Omega]$$

$$(151 + 1) r_c = 151 \times 29.15 = 4.4 \text{ k}$$

$$[(151 + 1) r_c \parallel R_B] = 4.4 \parallel 5.94 = 2.52 \text{ k}$$

$$Z_{out} = \left[\frac{(\beta+1) r_e \parallel R_B}{\beta+1} \right] \parallel R_E'$$


$$= 2.52 \text{ k} \parallel 10 \text{ k} \parallel R_E'$$

$$= \underline{1.08 \text{ k}} \quad \underline{28.71 \Omega}$$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{(\beta+1) r_e R_E'}{r_e [(\beta+1) r_e \parallel R_B] + (\beta+1) R_E'}$$

$$= \frac{(\beta+1) R_E'}{[(\beta+1) r_e \parallel R_B] + (\beta+1) R_E'}$$
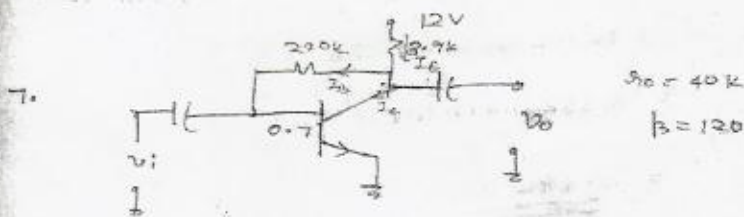
$$A_v = \frac{151 \times 1.9}{[2.52] + 151 \times 1.9} = \underline{0.991}$$



$$12 - I_E \times 3.9 \text{ k} - V_{CE} = 0$$

$$12 - 121 \times I_B \times 3.9 - 220 \times I_B - 0.7 = 0$$

$$11.3 = I_B (121 \times 2.9 + 220) \text{ k}$$

$$I_B = 0.163 \mu\text{A}$$

$$I_C = 1.96 \text{ mA}$$

$$I_E = 1.978 \text{ mA}$$

$$r_e = \frac{26}{1.978}$$

$$= \underline{13.16 \Omega}$$


$$Z_{in} = A_v = \frac{R_C'}{r_e} = \frac{8.91140}{13.16} = \underline{-3.553 \text{ k}}$$

$$R_{Bin} = \frac{R_B}{1 - A_V} = \frac{220}{1 + 269.9} = 0.812 \text{ k}$$

$$R_{Bout} = \frac{R_B}{1 - \frac{1}{A_V}} = \frac{220}{1 + \frac{1}{269.9}} = 219.18 \text{ k}$$

$$\begin{aligned} Z_{in} &= R_{Bin} \parallel (\beta + 1) r_e \\ &= 0.812 \text{ k} \parallel (101) \times 13.16 \Omega \\ &= 0.812 \text{ k} \parallel 1.572 \\ &= \underline{\underline{0.537 \text{ k}}} \end{aligned}$$
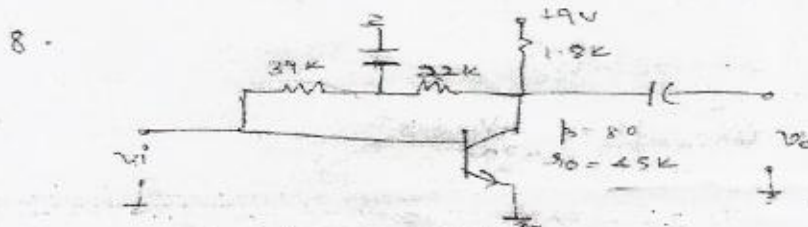
$$\begin{aligned} Z_{out} &= R_C' \parallel R_{Bout} \\ &= 3.9 \text{ k} \parallel 40 \text{ k} \parallel 219.18 \text{ k} \\ &= 3.55 \text{ k} \parallel 219.18 \text{ k} \\ &= \underline{\underline{3.49 \text{ k}}} \end{aligned}$$



$$9 - 81 \times I_B \times 1.8 - I_C \times 61 \text{ k} - 0.7 = 0$$

$$8.3 = I_B [81 \times 1.8 + 61]$$

$$I_B = \frac{8.3}{[81 \times 1.8 + 61]} = \underline{\underline{0.4 \mu\text{A}}}$$

$$I_E = 3.25 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = \underline{8 \Omega}$$

$$A_v = \frac{-R_c'}{r_e}$$

$$R_c' = 1.8 \text{ k} \parallel 45 \text{ k} = 1.73 \text{ k}$$

$$= \frac{-1.73 \text{ k}}{8}$$

$$= -216.25$$

$$R_{in} = \frac{22 \text{ k}}{1 + \beta} = 0.1 \text{ k}$$

$$R_{out} = \frac{22 \text{ k}}{1 + \beta} = 21.89 \text{ k}$$


$$A_v = \frac{-1.6}{8} = -200$$

$$Z_{in} = R_{in} \parallel (\beta + 1)r_e$$

$$= 0.1 \text{ k} \parallel 81 \Omega$$

$$= 0.1 \text{ k} \parallel 0.648 \text{ k}$$
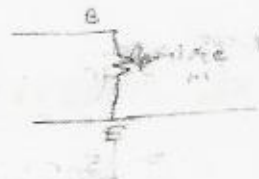
$$= 0.0866 \text{ k} = \underline{86.6 \Omega}$$



$$39 \text{ k} \parallel 0.648 \text{ k} = 0.637 \text{ k}$$

$$Z_{out} = R_c' \parallel R_{out}$$

$$= 1.73 \text{ k} \parallel 21.89 \text{ k}$$


$$= \underline{1.603 \text{ k}}$$

$$R_c = 22 \text{ k} \parallel 45 \text{ k}$$

$$= 1.66 \text{ k}$$

$$Z_{out} = 1.66 \text{ k} \parallel 45 \text{ k}$$


$$= \underline{1.6 \text{ k}}$$

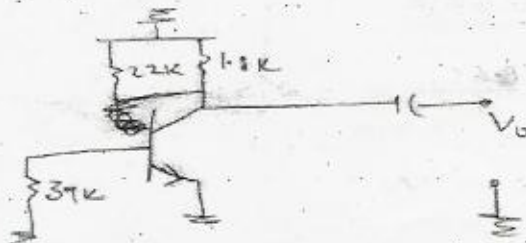

9. V_o/V_i , V_o/V_s , Z_i & Z_o

$$\beta_0 = \infty$$

$$\beta = 80$$

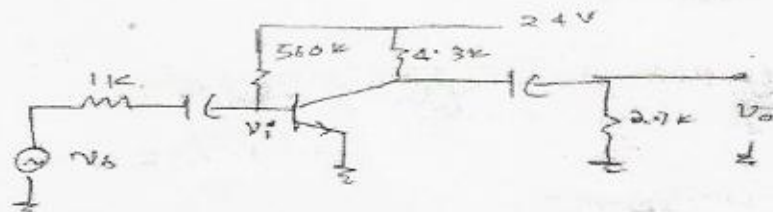

$$24 - 560 \times I_B - 0.7 = 0$$

$$23.3 = 560 \text{ k} I_B$$

$$I_B = 0.416 \text{ } \mu\text{A}$$

$$I_E = 3.37 \text{ mA}$$

$$r_e = \frac{V_T}{I_E} = 7.715 \Omega$$

$$Z_{in} = (R_B \parallel (\beta + 1)r_e)$$

$$= [560 \text{ k} \parallel 81 \times 7.715 \Omega]$$

$$= [560 \text{ k} \parallel 110625 \Omega]$$

$$= 0.624 \text{ k}\Omega$$

$$0.624 \text{ k} \parallel 1 \text{ k}$$

$$0.384 \text{ k}$$

$$Z_o = R_c' = 4.3 \text{ k} \parallel 2.7 \text{ k}$$

$$= 1.66 \text{ k}$$

$$\frac{V_o}{V_i} = -\frac{1.66 \text{ k}}{7.715} = -215.16$$

$$v_i = v_s \times \frac{0.624K}{0.624 + 1K}$$

$$\frac{v_i}{v_s} = 0.384$$

$$\frac{v_o}{v_s} = \frac{v_o}{v_i} \times \frac{v_i}{v_s} = -82.62$$

When R_s & R_L changed

$$Z_{in} = 0.624K \Omega$$

$$Z_{out} = 4.3K \parallel 5.6K$$


$$= 2.43K \Omega$$

$$A_v = \frac{v_o}{v_i} = \frac{-2.43K}{7.715} = -314.9$$

$$\frac{v_i}{v_s} = \frac{0.624K}{0.5 + 0.624} = 0.555$$

$$\frac{v_o}{v_s} = -174.87$$


100

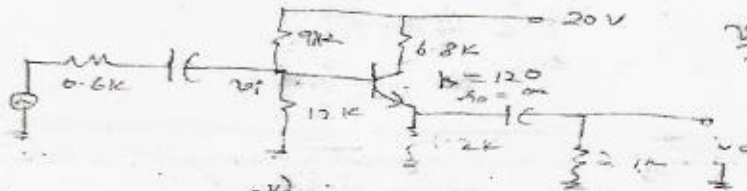

$$\frac{v_o}{v_i} = \frac{(1.2K \parallel 2.7K)}{20.537 + (1.2K \parallel 20K)} = 0.975$$

$$121 (20.54 + 1.2K \parallel 2.7K) = 103K \parallel (9K \parallel 12K)$$

$$48.5K \parallel 12K = 9.61K$$

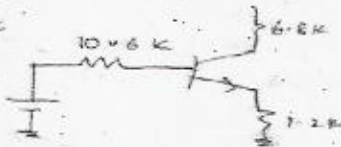

$$Z_{out} = R_c \parallel \left(\frac{0.6K \parallel 9K \parallel 12K}{\beta + 1} \right)$$

$$1.2K \parallel 2.7K = 24.5\Omega$$

$$2.33 - 10.6 \times Z_B - 0.7 - 121 \times J_B \times 1.2K = 0$$