

## TUTORIAL 5

1.

$$I_D = 0.75 \text{ mA}$$

$$\mu_n C_{ox} = 60$$

$$I_{n,ox} = 300 \mu\text{A}/\text{V}^2$$

$$V_A = 15 \text{ V}$$

$$R_D = 4.7 \text{ k}\Omega$$

$$g_m = \sqrt{2 \times I_D \times k_n' \frac{W}{L}}$$

$$= \sqrt{2 \times 0.75 \times 10^{-3} \times 300 \times 10^{-6} \times 60}$$

$$= 5.196 \text{ mA/V}$$

$$R_D = \frac{V_A}{I_D} = \frac{15}{0.75 \text{ mA}} = 20 \text{ k}\Omega$$

$$V_{OV} = \sqrt{\frac{2 I_D}{k_n' \frac{W}{L}}}$$

$$= \sqrt{\frac{2 \times 0.75 \text{ mA}}{300 \times 10^{-6} \times 60}}$$

$$V_{OV} = 0.288 \text{ V}$$

$$A_d = \frac{g_m R_D}{2}$$

$$= \frac{5.196 \times 10^{-3} \times 4.7 \times 10^3}{2}$$

$$= 12.2106$$

$$I = 0.375 \text{ mA}$$

$$3.67 \text{ mA/V}$$

$$40\%$$

$$0.2 \text{ V}$$

$$A_d = \frac{g_m R_D}{2}$$


$$= 3.67 \times 10^{-3}$$

$$\times (4.7 \text{ k}\Omega)$$

$$= 15.435$$

2.

$$a) A_d = 80$$

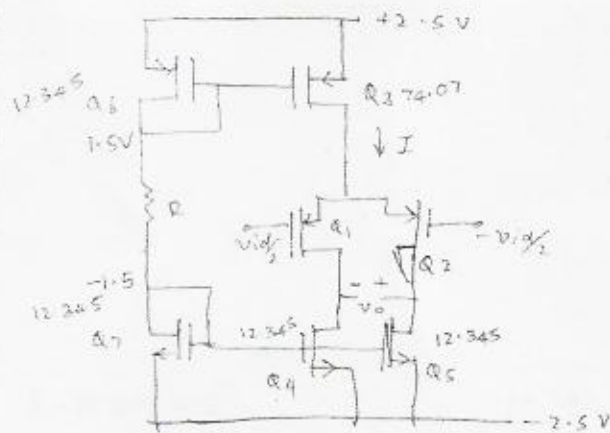

$$I_d = 80$$

$$I = 0.1 \text{ mA}$$

$$V_{GS} = -1.5 \text{ V}$$

$$V_{GS} = -1.5 \text{ V}$$

$$\mu_n C_{ox} = 90 \mu\text{A/V}^2$$

$$\mu_p C_{ox} = 30 \mu\text{A/V}^2$$

$$|V_{th}| = 0.7 \text{ V}$$

$$|V_A| = 20 \text{ V}$$

$$I = 0.1 \text{ mA}$$

$$0.1 \text{ mA} = \frac{1}{2} \times 30 \times 10^{-6} \times \left(\frac{W}{L}\right)_3 \times (1.5 - 2.5 - (-0.7))^2$$

$$0.1 \text{ mA} = \frac{1}{2} \times 30 \times 10^{-6} \times \left(\frac{W}{L}\right)_3 \times (-1 + 0.7)^2$$

$$0.1 \text{ mA} = \frac{1}{2} \times 30 \times 10^{-6} \times \left(\frac{W}{L}\right)_3 \times (-0.3)^2$$

$$\left(\frac{W}{L}\right)_3 = \frac{74.07}{24.031} = \left(\frac{W}{L}\right)_6$$

$$\text{Current thru } Q_5 = \frac{0.1}{2} = 0.05 \text{ mA}$$

$$0.05 \text{ mA} = \frac{1}{2} \times 90 \times 10^{-6} \times \left(\frac{W}{L}\right)_5 \times (-1.5 + 2.5 - 0.7)^2$$

$$\left(\frac{W}{L}\right)_5 = 12.345 = \left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_7 = 2 \left(\frac{W}{L}\right)_8$$

$$\left(\frac{W}{L}\right)_6 = 27.035$$

$$= 24.7$$

$$\frac{g_m R_d}{\beta} = 80$$

$$g_{m4}$$

$$= \frac{20}{0.05 \text{ mA}}$$

$$= 400 \text{ k}\Omega$$

$$g_m \times 200 \text{ k} = 80$$

$$g_m = 0.4 \text{ mA/V}$$

$$R_{01} = R_{02} = 400 \text{ k}\Omega$$


$$\sqrt{2 I k_p' (W/L)_1} = 0.4 \text{ mA/V}$$

$$2 I k_p' (W/L) = 0.16 \times 10^{-6}$$

$$(W/L)_1 = (W/L)_2 = \frac{0.16 \times 10^{-6}}{2 \times 0.05 \times 10^{-3} \times 30 \times 10^{-6}}$$

$$(W/L)_1 = (W/L)_2 = \boxed{53.33}$$
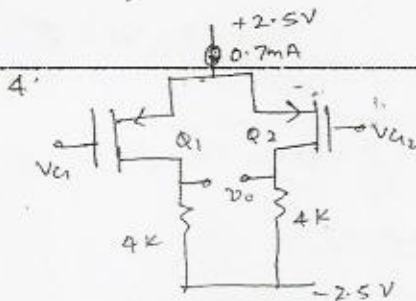
$$R = \frac{1.5 - (-1.5)}{0.001 \text{ mA}} = 30 \text{ k}\Omega$$



$$\mu_p \mu_n \cdot C_{ox} \cdot W/L = 4 \text{ mA/V}^2$$

$$R_{SS} = 25 \text{ k}\Omega$$

$$V_{ov} \quad g_m \quad A_d \quad A_{cm}$$

$$\text{CMRR} \text{ must } > 50\%$$

$$V_{ov} = \sqrt{\frac{2 I}{k_p' W/L}}$$

$$= \sqrt{\frac{2 \times 0.7}{4 \times 10^{-3}}} = 0.418 \text{ V}$$

$$g_m = \sqrt{2 I k_p' W/L}$$

$$= \sqrt{2 \times 0.7 \times 10^{-3} \times 4 \times 10^{-3}}$$

$$= 1.673 \text{ mA/V}$$

$$A_d = g_m R_d$$

$$= 1.673 \times 10^{-3} \times 4 \times 10^3$$

$$= 6.692$$


$$A_{cm} = \frac{\Delta R_d}{2 R_{SS}}$$

$$A_{cm} = \frac{1.5 \times 4 \text{ k}}{100 \times 2 \times 25 \text{ k}}$$

$$= 0.0012$$

$$\text{CMRR} = 6.692$$

5.

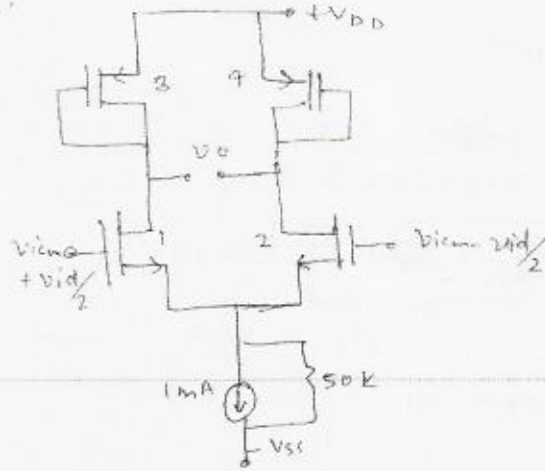

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 200$$

$$\left(\frac{W}{L}\right)_3 = 100 \quad \left(\frac{W}{L}\right)_4 = 120$$

$$k_n' = 100 \mu\text{A}/\text{V}^2$$

$$k_p' = 75 \mu\text{A}/\text{V}^2$$

$$V_{AN} = 5\text{V}, \quad V_{AP} = 0\text{V}$$

0.5 mA

$$g_{m3} = \sqrt{2 \times 0.5 \times 10^{-3} \times 75 \times 10^{-6} \times 100}$$

$$= 2.7386 \text{ mA/V}$$

$$r_{o3} = \frac{6}{0.5 \text{ mA}} = 12 \text{ k}$$

$$r_{o4} = \frac{6}{0.5 \text{ mA}} = 12 \text{ k}$$

$$g_{m4} = \sqrt{2 \times 0.5 \times 10^{-3} \times 75 \times 10^{-6} \times 120}$$

$$= 3 \text{ mA/V}$$

$$\left(\frac{1}{g_{m3}} \parallel r_{o3}\right) = \left(\frac{1}{2.7386 \text{ mA/V}} \parallel 12 \text{ k}\right)$$

$$= (0.365 \text{ k} \parallel 12 \text{ k})$$

$$= 0.354 \text{ k}$$

$$\left(\frac{1}{g_{m4}} \parallel r_{o4}\right) = (0.333 \text{ k} \parallel 12 \text{ k})$$

$$= 0.324 \text{ k}$$

$$A_d = g_m R_{d1} - (-g_m R_{d2})$$

$$= g_m \left( R_{d1} + R_{d2} \right)$$

$$g_m = \sqrt{2 \times 0.5 \times 10^{-3} \times 100 \times 10^{-6} \times 200}$$

$$= 4.47 \times 10^{-3} \text{ A/V}$$

$$= 4.47 \times 10^{-3} \times \left( \frac{0.354}{2} + \frac{0.324}{2} \right)$$


$$= 1.51533$$

$$A_{cm} = \frac{\Delta R_d}{2R_u}$$


$$= \frac{0.030K}{2 \times 50K}$$

$$= 3 \times 10^{-4}$$
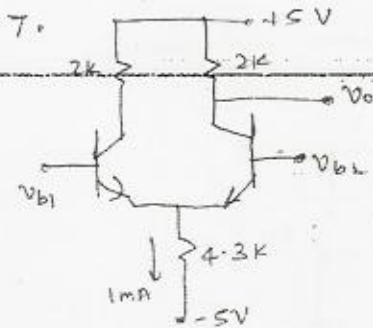
$$CMRR = \frac{1.5153}{3 \times 10^{-4}} = 74.067 \text{ dB}$$



a)

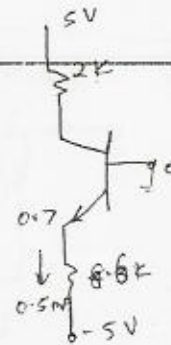

$$A_{cm} \approx r_e = \frac{26}{0.5} = 52 \Omega$$

$$v_{id} - v_{sd} = v_{id} \times \left[ \frac{-R_c}{2} \frac{1}{r_e} \right] - \left[ -v_{id} \frac{1}{2} \left( \frac{-R_c}{r_e} \right) \right]$$

$$v_{id} - v_{sd} = \frac{v_{id}}{2} \left[ -\frac{R_c}{r_e} - \frac{R_c}{r_e} \right] \quad A_d = \frac{R_c}{r_e} \text{ (single-ended)}$$

$$= \frac{2K}{102 \Omega} = 19.60$$

$$b) \quad A_{cm} = \frac{R_c}{2R_E}$$

$$= \frac{2K}{2 \times 8.6K}$$

$$= 0.2326$$

$$c) \quad CMRR = \frac{19.60}{0.2326} = 84.26 \text{ dB}$$

$$= 38.513$$

$$d) v_{em} = 0.2326 (0.1 \sin 2\pi 60t)$$


$$= 0.2326 \sin 2\pi 60t$$

$$v_{od} = 19.6 \times 2 \times 0.005 \sin 2\pi 1000t$$

$$= 0.196 \sin 2\pi 1000t$$

$$v_o = 0.2326 \sin 2\pi 60t + 0.196 \sin 2\pi 1000t$$

Titel 3) - Emitter folgen

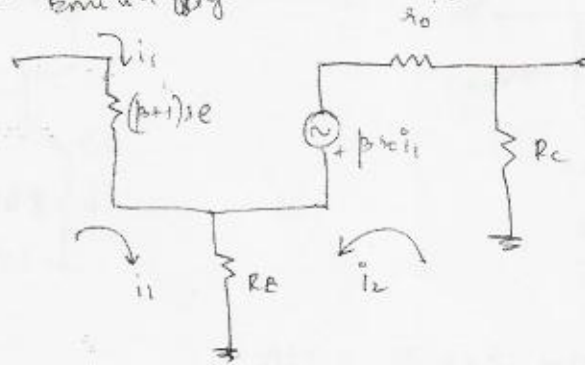

$$i_2 (R_C + R_E + r_o) = \beta r_o i_1$$

$$i_2 = \frac{\beta r_o}{R_C + R_E + r_o} i_1$$

$$= \frac{\beta}{1 + \frac{R_E + R_C}{r_o}} i_1$$

$$i_2 = \beta' i_1$$

$$v_o = -i_2 R_C$$


$$= -\beta' i_1 R_C$$

$$v_o = -\beta' R_C \frac{v_{in}}{R_{in}}$$


$$\frac{v_o}{v_{in}} = \frac{-\beta' R_C}{(\beta+1)r_e + R_E + \beta' R_C}$$

$$\frac{v_o}{v_{in}} = -\frac{R_c}{R_e}$$

3.

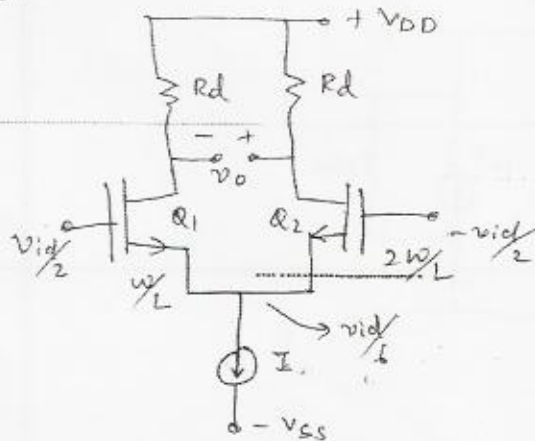

6.

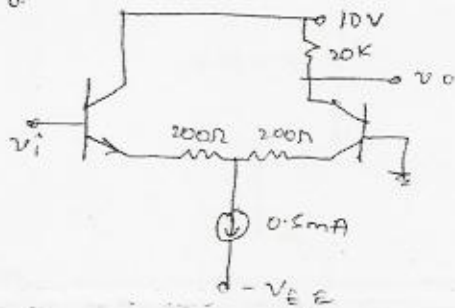

$$R_c = 20K$$

$$r_e = 100\Omega$$

$$R_e = 200 + 200 + 200 = 600$$


$$A_d = \frac{R_c}{R_e} = 33.33$$

$$R_{in} = (\beta + 1)(r_e + 200 + 200 + 200)$$

$$= 101(600)$$

$$= \underline{\underline{60.6k\Omega}}$$

8 >

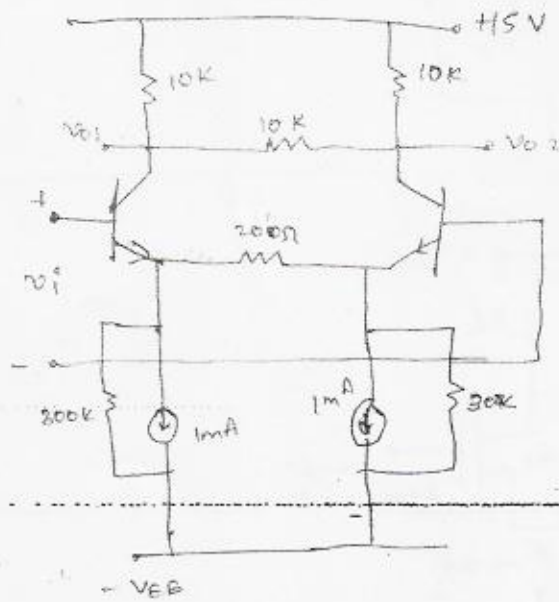

$A_d, R_{id}, A_{cm} \& R_{icm}$


$A_d = 3.33K$

$R_E = 126 \Omega$

$= 26.428$

$A_{id} = \frac{\text{Total } R_C}{\text{Total } R_E} = \frac{5.667}{200 + 52}$

$= 26.458$

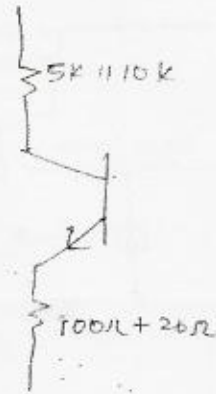


$R_{id} \text{ cm} = \frac{10K}{300K} = 0.0333$

(10k is redundant)

$R_{icm} = (\beta + 1)R_E + R_C + R_E \beta'$

$\approx R_E \beta'$

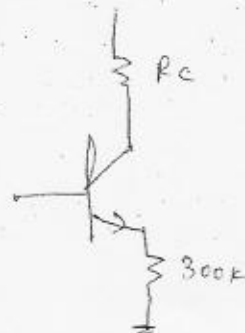$\approx R_E \times \frac{\beta}{1 + \frac{R_E}{\beta_0}}$





$$V_A = 100 \text{ V} \quad \beta = 100$$

$$R_{icm} = \frac{\beta (R_E \parallel r_{o1})}{2}$$

$$= 50 \times (300 \text{ k} \parallel 100 \text{ k})$$

$$= 50 \times (300 \text{ k} \parallel 100 \text{ k})$$

$$= ~~112.5 \text{ k}\Omega~~$$

$$= \underline{\underline{3.75 \text{ M}\Omega}}$$

$$I_0 = \frac{100 \text{ V}}{100 \text{ k}\Omega}$$

$$R_{id} = 2(\beta + 1)(200 \Omega + 52 \Omega)$$


$$= 2 \times 101 \times 252 \Omega$$

$$= \underline{\underline{50.9 \text{ k}\Omega}}$$

$$= 201 \times (200 + 52) \Omega$$

$$= 101 \times (200 + 52)$$
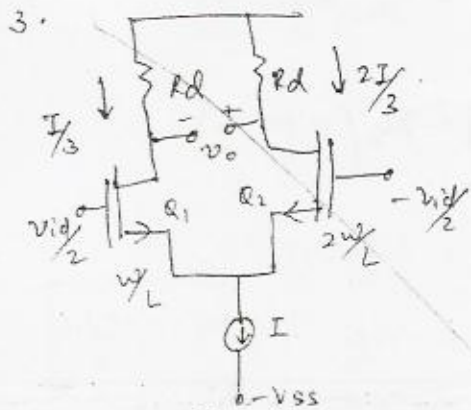
$$= \underline{\underline{25.452 \text{ k}\Omega}}$$



$$I_2 = 2I_1$$

$$I_1 + 2I_1 = I$$

$$I_1 = I/3$$

$$I_{d1} = I/3 \quad I_{d2} = 2I/3$$

$$b) \quad V_{ov} = \sqrt{\frac{2I}{kn' \frac{W}{L}}}$$

$$= \sqrt{\frac{2I}{3 kn' \frac{W}{L}}}$$

c)  $A_{d0}$

$$v_o = -\frac{v_{id}}{2} (-g_{m2} R_d) - \frac{v_{id}}{2} (-g_{m1} R_d)$$

$$v_o = v_{id} \left[ \frac{g_{m2} R_d}{2} + \frac{g_{m1} R_d}{2} \right] \quad g_{m2} = 2g_{m1}$$

$$\frac{v_o}{v_{id}} = R_d (g_m + a) \quad \dots$$

$$g_{m1} = \frac{2I_{d1}}{V_{ov}}$$

$$a \quad A_d = \frac{3 R_d \times 2 I_{d1}}{2 V_{ov}}$$

$$I_{d1} = \frac{I}{3}$$

$$= \frac{3 R_d \times 2 I}{2 V_{ov}} = \boxed{\frac{I R_d}{V_{ov}}}$$

$$i_1 = g_{m1} \left( \frac{v_{id}}{2} - v_s \right)$$

$$i_2 = -g_{m2} \left( -\frac{v_{id}}{2} - v_s \right)$$

$$g_{m2} \left( \frac{v_{id}}{2} + v_s \right) = g_{m1} \left( \frac{v_{id}}{2} - v_s \right)$$

$$2 g_{m2} \left( \frac{v_{id}}{2} + v_s \right) = g_{m1} \left( \frac{v_{id}}{2} - v_s \right)$$

$$v_{id} + 2v_s = \frac{v_{id}}{2} - v_s$$

$$3v_s = -\frac{v_{id}}{2}$$

$$v_s = -\frac{v_{id}}{6}$$

9.

NMOS

$$V_{ov} = 0.25 \text{ V}$$

$$V_{An} = 8 \text{ V}$$

$$g_{m1} = 0.075 \text{ PF}$$

$$C_L = 0.15 \text{ PF}$$

$$I = 0.4 \text{ mA}$$

$$g_n = \frac{2I}{V_{ov}} = \frac{2 \times 0.4 \text{ mA}}{0.25} = 3.2 \text{ mA/V}$$

PMOS

$$V_{ov} = 0.4 \text{ V}$$

$$V_{Ap} = 8 \text{ V}$$

$$g_p = \frac{2I}{V_{ov}}$$

$$= \frac{2 \times 0.4 \text{ mA}}{0.4}$$

$$= 2 \text{ mA/V}$$

o . . . o

$$R_o = 40411.802$$

$$= 10 \text{ k}\Omega$$

$$A_d = \frac{A_o}{2} = g_m \times R_o$$

$$= 3.2 \times 10^{-3} \times 10 \times 10^3$$

$$= 32$$

$$A_{cm} = \frac{1}{2 g_m R_u} \quad R_u \text{ assume } 100 \text{ k}\Omega$$

$$= \frac{1}{2 \times 3.2 \times 10^{-3} \times 100 \times 10^3}$$

$$= 2.5 \times 10^{-3}$$

$$CMRR = \frac{32}{2.5 \times 10^{-3}} = 82.144 \text{ dB}$$

$$b_{p1} = \frac{g_m}{2\pi C_m} = \frac{g_m}{2\pi C_m}$$

$$= \frac{2 \times 10^{-3}}{2\pi \times 0.075 \text{ pF}}$$


$$= 4.244 \text{ GHz}$$

$$b_z = 2 \times b_{p1} = 8.488 \text{ GHz}$$

$$b_{p2} = \frac{1}{2\pi R_o C_L} = \frac{1}{2\pi \times 10 \text{ k}\Omega \times 0.15 \times 10^{-12}}$$

$$= 106.103 \text{ MHz}$$

10

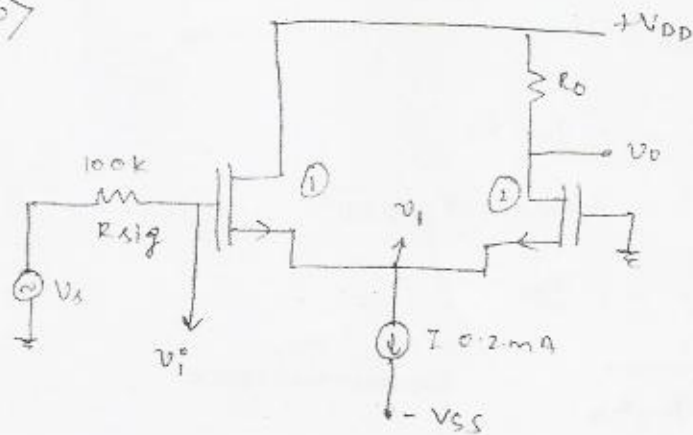

Stg ① is CD config

$$A_{\text{gain}} = \frac{R_s}{R_s + \frac{1}{g_m}}$$

$R_s$  is impedance looking into source of ②

$$A_{\text{gain}} = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

Given:  $V_{ov} = 0.25V$      $I = 0.2mA$

$$\therefore g_m = \frac{2 \times 0.1}{0.25} = 0.8 \text{ mA/V}$$

$$g_{m1} = g_{m2}$$

$$\therefore A_{\text{gain}} = \frac{1}{2} \Rightarrow \frac{v_1}{v_i} = \frac{1}{2}$$

$$\boxed{v_1 = \frac{v_i}{2}}$$

Now gain of ②. CG config

$$A_{\text{gain}} = g_m R_d$$

$$\frac{v_o}{v_1} = g_m R_d$$

$$\frac{v_o}{v_i} = g_m R_d$$


$$\boxed{\frac{v_o}{v_i} = g_m R_d = 12}$$

Since  $Z_{in}$  of MOSFET =  $\infty$

$$\frac{V_o}{V_i} = \frac{V_o}{V_i} = 12$$


At high frequency:

Eqt:

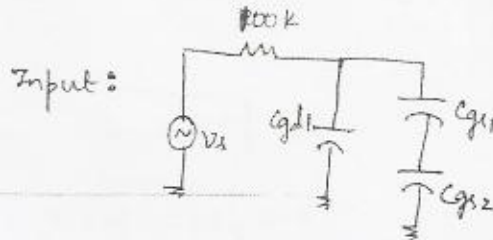

$$C_{gs} = 1pF$$


$$C_{gd} = 0.5pF$$

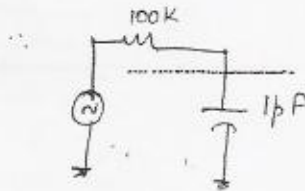

$$f_{p1} = \frac{1}{2\pi \times 100k \times 1 \times 10^{-12}}$$

$$= \underline{\underline{1.59 MHz}}$$

output:

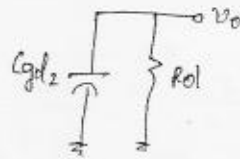


$$f_{p2} = \frac{1}{2\pi \times 30k \times 0.5 \times 10^{-12}}$$

$$= \underline{\underline{10.6 MHz}}$$

No zeroes exist only poles

$$|b_H| \approx 1.6 MHz$$

3)

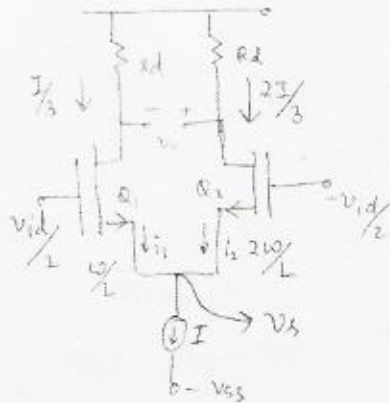

$$I_1 + I_2 = I$$

$$I_1 + 2I_1 = I$$

$$3I_1 = I$$

$$I_1 = \frac{I}{3}$$

$$g_m = \sqrt{2 I_0 k_n' \frac{W}{L}}$$

$$g_{m1} = \sqrt{2 \times \frac{I}{3} \times k_n' \times \frac{W}{L}}$$

$$g_{m2} = \sqrt{2 \times 2 \frac{I}{3} \times k_n' \times 2 \frac{W}{L}}$$

$$\Rightarrow g_{m2} = 2g_{m1}$$

$$A_d = \frac{\text{Total resistance in drain loop}}{\text{Total resistance in source loop}}$$

$$= \frac{2R_d}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} = \frac{2R_d}{\frac{1}{g_{m1}} + \frac{1}{2g_{m1}}}$$

$$V_{ov1} = \sqrt{\frac{2 I_0}{k_n' \frac{W}{L}}} = \sqrt{\frac{2 I}{3 k_n' \frac{W}{L}}} \quad = \frac{4 R_d}{\frac{1}{g_{m1}} \times 3} = \boxed{\frac{4}{3} g_{m1} R_d}$$

$$V_{ov2} = \sqrt{\frac{2 \times 2 I}{3 \times k_n' \times 2 \frac{W}{L}}} = \sqrt{\frac{2 I}{3 k_n' \frac{W}{L}}} \Rightarrow \boxed{V_{ov2} = V_{ov1}}$$

$$A_d = \frac{4}{3} g_{m1} R_d$$

$$g_{m1} = \frac{2 \times I}{3 \times V_{ov}}$$

$$\boxed{A_d = \frac{4 \times 2 I}{3 \times 3 V_{ov}} R_d = \frac{8}{9} \frac{I R_d}{V_{ov}}}$$

$$2 \times \frac{v_s}{2} = \frac{1.125}{2.22 \times 10^{-3}}$$

$$\underline{3.125} \quad 35.22\%$$

$$P_{\text{max}} = \frac{36}{8} = 4.5 \text{ W}$$

$$P_0 = 0.7 \text{ W (approx)}$$

To prove  $v_s = \frac{v_{id}}{6}$

$$i_1 = g_{m1} \left( \frac{v_{id}}{2} - v_s \right) \quad (\text{AC current})$$

$$i_2 = -g_{m2} \left( -\frac{v_{id}}{2} - v_s \right)$$

$$i_1 = i_2$$

$$g_{m1} \left( \frac{v_{id}}{2} - v_s \right) = -2g_{m2} \left( -\frac{v_{id}}{2} - v_s \right)$$

$$\frac{v_{id}}{2} - v_s = v_{id} + 2v_s$$

$$-3v_s = \frac{v_{id}}{2}$$

$$\boxed{v_s = -\frac{v_{id}}{6}}$$